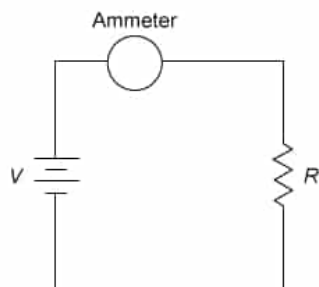


A battery of unknown voltage V is connected to a resistor R and an ammeter as shown.




Researchers change the value of R and record the reading of the ammeter each time. The value of V can best be determined from which of the following?

- ☐ A. The slope of a graph of current as a function of R [27%]
- ☒ B. The slope of a graph of current as a function of $1/R$ [50%]
- ☐ C. The y-intercept of a graph of current as a function of R [14%]
- ☐ D. The y-intercept of a graph of current as a function of $1/R$ [7%]

Correct

50% answered correctly

Explanation:

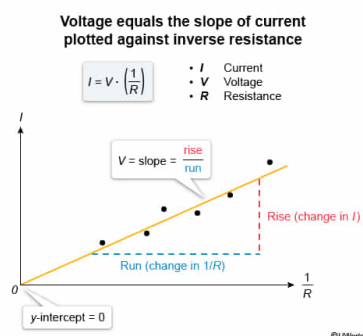

Ohm's law states that the current I between two points in a closed circuit is **directly proportional** to the **voltage** V between those two points and **inversely proportional** to the resistance R :

$$I = \frac{V}{R}$$

In this question, researchers are trying to determine the unknown V of a battery by using an ammeter to measure the current when R changes. If the data for the current are plotted on the y-axis of a graph (as the y-variable) and the data for the *inverse* of resistance $\frac{1}{R}$ are plotted on the x-axis (as the x-variable), then Ohm's law can be expressed as a **linear function** in **slope (m)-intercept (b) form**:

$$y = m \cdot x + b$$

$$\downarrow$$

$$I = V \cdot \left(\frac{1}{R}\right) + 0$$

When Ohm's law is expressed in this way, the slope of the line is equal to V and the y-intercept is zero. Therefore, the value of V can be determined from the slope of the graph of current as a function of $\frac{1}{R}$.

(Choice A) The graph of current as a function of resistance would yield an **inverse relationship** curve rather than a straight line with a slope that can be calculated as function of R .

(Choices C and D) The y-intercept of a graph of I versus R (or I versus $\frac{1}{R}$) would give the value of the current only when R (or $\frac{1}{R}$) equals zero. Therefore, the y-intercept does not yield any information about the voltage of the battery.

Educational objective:

Ohm's law can be expressed as a linear relationship between the current and the inverse of resistance, with voltage equal to the slope of the line.